

University of Victoria
Department of Computer Science
COMPUTER SCIENCE 355

Fall 2023- ASSIGNMENT 2


Due Thursday, November 9, 2023 by 11:59PM on Brightspace

Show all the steps in your work to receive marks; the final solution only will not get credit.

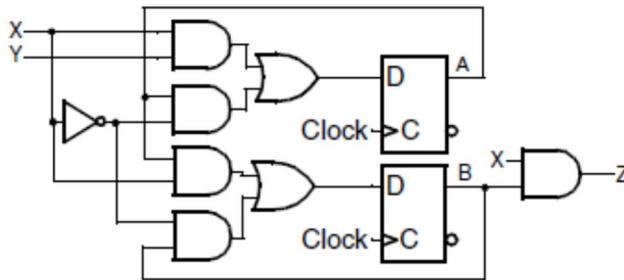1. [6 marks] A sequential circuit with two *D* flip-flops *A* and *B*, two inputs *X* and *Y*, and one output *Z* is specified by the following input equations:

$$D_A = \bar{X}A + XY, D_B = \bar{X}B + XA, Z = XB$$


- Draw the logic diagram of the circuit.
- Derive the state table.
- Derive the state diagram.





Present state		Inputs		Next state		Output
A	B	X	Y	A	B	Z
0	0	0	0	0	0	0
0	0	0	1	0	0	0
0	0	1	0	0	0	0
0	0	1	1	1	0	0
0	1	0	0	0	1	0
0	1	0	1	0	1	0
0	1	1	0	0	0	1
0	1	1	1	1	0	1
1	0	0	0	1	0	0
1	0	0	1	1	0	0
1	0	1	0	0	1	0
1	0	1	1	1	1	0
1	1	0	0	1	1	0
1	1	0	1	1	1	0
1	1	1	0	0	1	1
1	1	1	1	1	1	1

S0 - 00
S1 - 01
S2 - 10
S3 - 11

 Format: XY/Z (X = unspecified)
0X/0, X0/0



  2. [4 marks] For a T Flip Flop, the inputs, T and Clk are as given in the timing diagram below. Complete the timing diagram by drawing the Q output.



T-Flip Flop $Q^+ = \bar{T}Q + T\bar{Q} = T \oplus Q$

T	Q	Q ⁺
0	0	0
0	1	1
1	0	1
1	1	0

3. [6 marks] A combinational circuit is defined by the following two Boolean functions:

$$F_1 = \overline{X + Z} + XYZ$$

$$F_2 = \overline{X + Z} + \overline{X}YZ$$

- Design the circuit with a decoder and external OR gates
- Design the circuit with multiplexers. Choose the right size multiplexer.

$$F_1 = \overline{X + Z} + XYZ = \overline{X} \overline{Z} + XYZ = \overline{X} \overline{Z} \cdot (Y + \overline{Y}) + XYZ$$


$$= \overline{X} Y \overline{Z} + \overline{X} \overline{Y} \overline{Z} + XYZ$$

$$\begin{matrix} 0 & 1 & 0 & & 0 & 0 & 0 & & 1 & 1 & 1 \end{matrix}$$

$$F_2 = \overline{X + Z} + \overline{X}YZ = \overline{X} Y \overline{Z} + \overline{X} \overline{Y} \overline{Z} + \overline{X} Y Z$$

$$\begin{matrix} 0 & 1 & 0 & & 0 & 0 & 0 & & 0 & 1 & 1 \end{matrix}$$


a)

 

b)


x	y	z	F ₁	F ₂
0	0	0	0 = \overline{Z}	1 = \overline{Z}
0	0	1	0 = \overline{Z}	1 = 1
0	1	0	1 = \overline{Z}	1 = 1
0	1	1	0 = 0	0 = 0
1	0	0	0 = 0	0 = 0
1	0	1	0 = 0	0 = 0
1	1	0	0 = \overline{Z}	0 = 0
1	1	1	1 = 1	0 = 0

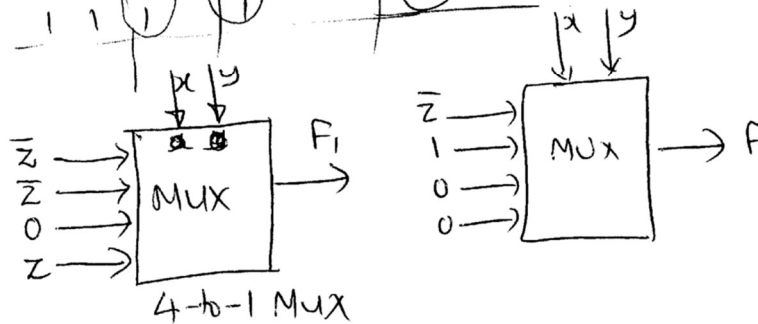n variable
(n-1) bit select
 $2^{(n-1)}$ line Mux



4. [4 marks] For the following JK flip flop, complete the timing diagram.

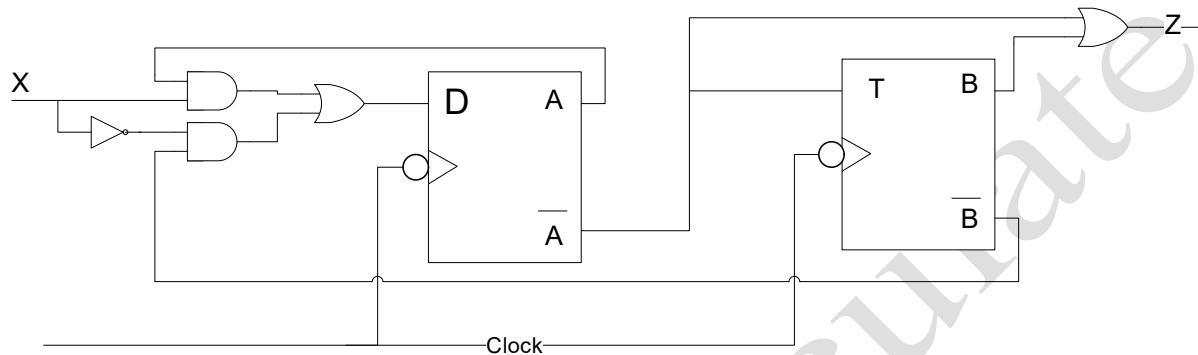5. [6 Marks] For the following circuit with input X and output Z, draw a state diagram describing its behaviour:



1) Input/output equations for FF

For A: $D_A = XA + \bar{X}\bar{B}$

For B: $T_B = \bar{A}$

o/p equation
 $Z = B + \bar{A}$ Independent of X

2) Next State equations

$A^+ = D_A = XA + \bar{X}\bar{B}$

$B^+ = \bar{T}_B \cdot B + T_B \cdot \bar{B} = AB + \bar{A}\bar{B}$

3) Next State Maps

Map for A^+ :

AB	00	01	11	10
X=0	1	1	0	1
X=1	0	0	1	1

Map for B^+ :


AB	00	01	11	10
X=0	1	1	1	1
X=1	1	1	1	1

Map for Z:

AB	00	01	11	10
X=0	1	1	1	1
X=1	1	1	1	1

4) State Table from maps

A	B	Next State		Output Z	
		X=0 $A^+ B^+$	X=1 $A^+ B^+$	X=0	X=1
0	0	1	0	1	1
0	1	0	0	0	1
1	1	0	1	1	1
1	0	1	0	1	0

 


6. [6 marks] Design a counter that goes through the sequence:

1 4 3 5 2 7 and repeat

using a D flip flop for A, a JK flip flop for B, and a T flip flop for C. Use bit A as the least significant bit (LSB) and C as the most significant bit (MSB).

7. [6 marks] A Universal Serial Bus (USB) communication link requires a circuit that produces the sequence 00000001. You are to design a synchronous sequential circuit that starts producing this sequence for input $E = 1$. Once the sequence starts, it completes. If $E = 1$, during the last output in the sequence, the sequence repeats. Otherwise, if $E = 0$, the output remains constant at 1.

 - (a) Draw the state diagram for the circuit.
 (b) Find the state table and make a state assignment.
 (c) Design the circuit using D flip-flops and logic gates. A reset should be included to place the circuit in the appropriate initial state at which E is examined to determine if the sequence of constant 1s is to be produced.



Present state $D_2D_1D_0$	Next State For Input		Output Z
	$E=0$	$E=1$	
000	001	001	0
001	010	010	0
010	011	011	0
011	100	100	0
100	101	101	0
101	110	110	0
110	111	111	0
111	111	000	1

The state assignment could be different. E. g., state 7 could be 000 with state 0 001. This would permit use of R inputs on the D flip-flops for RESET.

